

Lab 5: Martin Kousal

Link to your **Digital-electronics-2** GitHub repository:

<https://github.com/mkousal/Digital-electronics-2>

7-segment library

1. In your words, describe the difference between Common Cathode and Common Anode 7-segment display.
 - **CC SSD** - displays with common cathode have shared cathode between all segments, single segments are turned on with logical 1 (positive voltage). If we want to turn one digit on, we must ground this cathode.
 - **CA SSD** - displays with common anode have shared anode between all segments, single segments are turned on with logical 0 (grounded). If we want to turn digit on, we must provide supply voltage to this anode.
2. Code listing with syntax highlighting of two interrupt service routines (**TIMER0_OVF_vect**, **TIMER0_OVF_vect**) from counter application with at least two digits, ie. values from 00 to 59:

```
volatile uint8_t cnt[] = {0,0,0,0};

/* Interrupt service routines -----*/
/*****
 * Function: Timer/Counter1 overflow interrupt
 * Purpose: Increment decimal counter value and display it on SSD.
 *****/
ISR(TIMER1_OVF_vect)
{
    cnt[0]++;

    if (cnt[0] == 10)
    {
        cnt[0] = 0;
        cnt[1]++;
    }
    if (cnt[1] == 6)
    {
        cnt[1] = 0;
        cnt[2]++;
    }
    if (cnt[2] == 10)
    {
        cnt[2] = 0;
        cnt[3]++;
    }
    if (cnt[3] == 6)
    {

```

```

        cnt[3] = 0;
    }
}


```

```

/*****
 * Function: Timer/Counter0 overflow interrupt
 * Purpose: Display tens and units of a counter at SSD.
 *****/
ISR(TIMER0_OVF_vect)
{
    static uint8_t pos = 0;
    static int8_t dir = 1;
    if (pos != 2)
        SEG_update_shift_regs(cnt[pos], pos, 0);
    else
        SEG_update_shift_regs(cnt[pos], pos, 1);
    pos += dir;
    if (pos == 3)
        dir = -1;
    if (pos == 0)
        dir = 1;
}

```

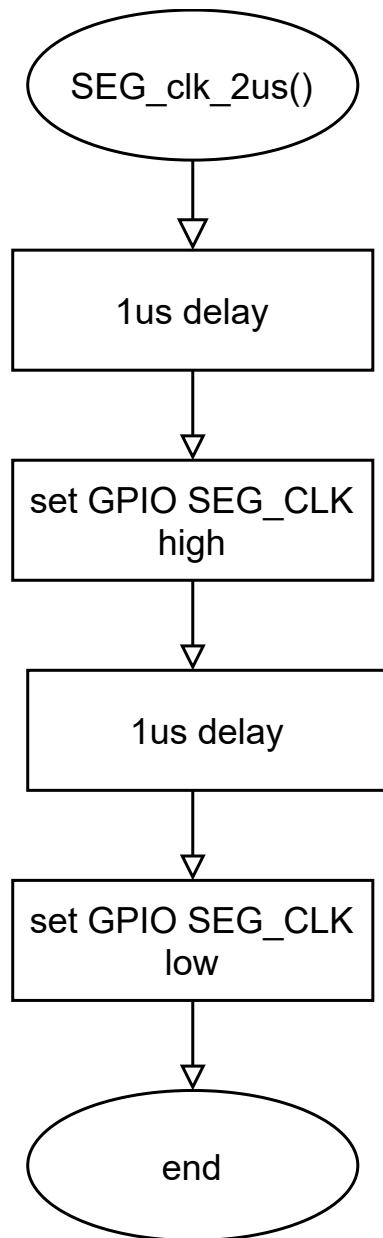3. Flowchart figure for function `SEG_clk_2us()` which generates one clock period on `SEG_CLK` pin with a duration of 2 us. The image can be drawn on a computer or by hand. Use clear descriptions of the individual steps of the algorithms.



Kitchen alarm

Consider a kitchen alarm with a 7-segment display, one LED and three push buttons: start, +1 minute, -1 minute. Use the +1/-1 minute buttons to increment/decrement the timer value. After pressing the Start button, the countdown starts. The countdown value is shown on the display in the form of mm.ss (minutes.seconds). At the end of the countdown, the LED will start blinking.

1. Scheme of kitchen alarm; do not forget the supply voltage. The image can be drawn on a computer or by hand. Always name all components and their values.

